

Resonant Frequency = _____ Hz


$XL =$ _____ Ohms $IL =$ _____ amps

$XC =$ _____ Ohms $IC =$ _____ amps

$Z =$ _____ Ohms $Ir =$ _____ amps

Phase Angle = (+/-) _____ degrees

The circuit is (Inductive/Capacitive)

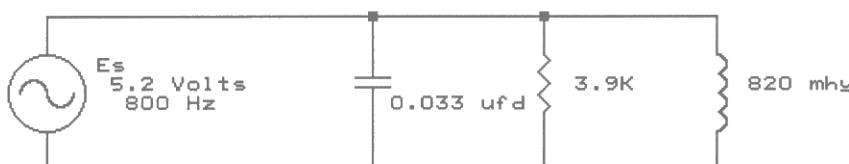

Resonant Frequency = _____ Hz


$XL =$ _____ Ohms $IL =$ _____ amps

$XC =$ _____ Ohms $IC =$ _____ amps

$Z =$ _____ Ohms $Ir =$ _____ amps

Phase Angle = (+/-) _____ degrees

The circuit is (Inductive/Capacitive)

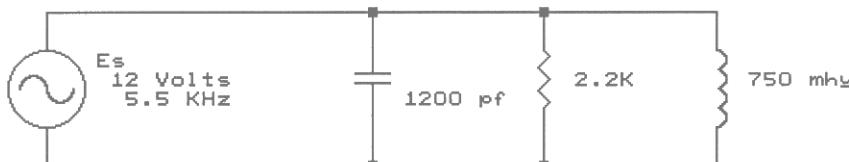

Resonant Frequency = _____ Hz


$XL =$ _____ Ohms $IL =$ _____ amps

$XC =$ _____ Ohms $IC =$ _____ amps

$Z =$ _____ Ohms $Ir =$ _____ amps

Phase Angle = (+/-) _____ degrees

The circuit is (Inductive/Capacitive)

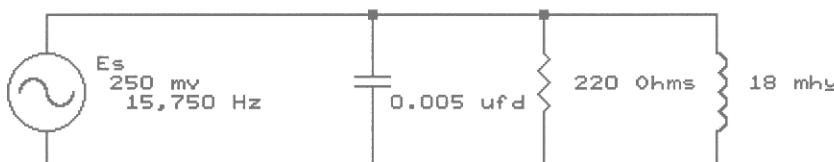

Resonant Frequency = _____ Hz

$XL =$ _____ Ohms $IL =$ _____ amps

$XC =$ _____ Ohms $IC =$ _____ amps

$Z =$ _____ Ohms $Ir =$ _____ amps

Phase Angle = (+/-) _____ degrees

The circuit is (Inductive/Capacitive)

Parallel_Z - ddf		
Size	Document Number	REV
A	Practice.004	
Date:	July 12, 1992	Sheet of