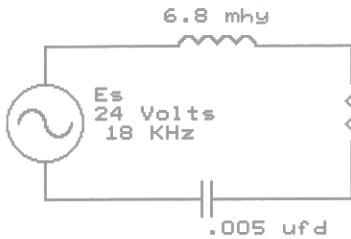


$XL = \underline{\hspace{2cm}}$ Ohms $EL = \underline{\hspace{2cm}}$ Volts Resonant Freq = $\underline{\hspace{2cm}}$
 $XC = \underline{\hspace{2cm}}$ Ohms $EC = \underline{\hspace{2cm}}$ Volts
 $Z = \underline{\hspace{2cm}}$ Ohms $ER = \underline{\hspace{2cm}}$ Volts

Phase Angle = $(+/-) \underline{\hspace{2cm}}$ degrees


The circuit is (Inductive/Capacitive)



$XL = \underline{\hspace{2cm}}$ Ohms $EL = \underline{\hspace{2cm}}$ Volts Resonant Freq = $\underline{\hspace{2cm}}$
 $XC = \underline{\hspace{2cm}}$ Ohms $EC = \underline{\hspace{2cm}}$ Volts
 $Z = \underline{\hspace{2cm}}$ Ohms $ER = \underline{\hspace{2cm}}$ Volts

Phase Angle = $(+/-) \underline{\hspace{2cm}}$ degrees


The circuit is (Inductive/Capacitive)

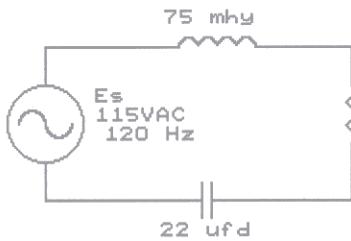

$XL = \underline{\hspace{2cm}}$ Ohms $EL = \underline{\hspace{2cm}}$ Volts Resonant Freq = $\underline{\hspace{2cm}}$
 $XC = \underline{\hspace{2cm}}$ Ohms $EC = \underline{\hspace{2cm}}$ Volts
 $Z = \underline{\hspace{2cm}}$ Ohms $ER = \underline{\hspace{2cm}}$ Volts

Phase Angle = $(+/-) \underline{\hspace{2cm}}$ degrees

The circuit is (Inductive/Capacitive)

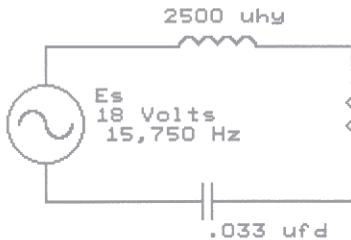

$XL = \underline{\hspace{2cm}}$ Ohms $EL = \underline{\hspace{2cm}}$ Volts Resonant Freq = $\underline{\hspace{2cm}}$
 $XC = \underline{\hspace{2cm}}$ Ohms $EC = \underline{\hspace{2cm}}$ Volts
 $Z = \underline{\hspace{2cm}}$ Ohms $ER = \underline{\hspace{2cm}}$ Volts

Phase Angle = $(+/-) \underline{\hspace{2cm}}$ degrees

The circuit is (Inductive/Capacitive)

| Series_Z | | |
|----------|-----------------|---|
| Size | Document Number | REV |
| A | Practice.003 | |
| Date: | July 12, 1992 | Sheet of |