

Digital *Disciplines:

* *Discipline:* “A rigorous way or procedure of doing a task “

Key Phrases & Thoughts:

- The “**Function**” of a SPST_NO switch would be to **Close**
- The “**Function**” of a SPST_NC switch would be to **Open**
- The “**Function**” of a Transistor may be to **conduct** a signal line **toward ground**, or the “**Function**” of a Transistor may be to **conduct** a signal line **toward a supply voltage**, or the “**Function**” of a Transistor may be to allow a signal line to be **released**.

- Think “**Function**” not “**Gate**”
- “**Only**” Gate vs. And Gate
- “**Any**” Gate vs. Or Gate
- Think “**Low**” when you see a Bubble
- “When you change **everything**, you change **nothing**”
(DeMorgan’s Law simplified)
- “**Gate Transform**”
- “**Direct Implementation**” vs. “**Direct Expression**”
- “**Forced**” vs. “**Maybe**” Conditions

- Dynamic Signal Analysis
 - “**Enable**” vs. “**Inhibit**”
 - “**Active**” vs. “**Resting**”
 - “**Inverted Output**” vs. “**Non-Inverted**”

- Totem-Pole Considerations (Outputs)
 - “**Sink-Current**” (Active Pull-Down) 10 ma (10x the Source-Current)
 - “**Source-Current**” (Active Pull-Up) 1 ma
(Never drive LED’s with the Source-Current)

- Input Thresholds (Each “Family” has it’s own specs!)
 - Voltage requirements
 - Lower-Threshold
 - Upper-Threshold
 - Current requirements
 - Lower-Threshold
 - Upper-Threshold
 - Resistance requirements
 - Lower-Threshold
 - Upper-Threshold