



Z_Ref1 = ____

Formulas:

$R_{st} = (DC_RL + ac_r1 + R_e)$
 $I_c = E_{cc} / R_{st}$
 $E_{ce} = I_c * ac_r1$
 $R1 = SI * R_{st}$
 or:
 $R1 = (E_{cc} - E_{R2}) / (I_{R2} + I_b)$

 $R2 = R2 * R_e / (DC_RL + ac_r1)$
 or:
 $R2 = SI * R_e$
 or:
 $R2 = E_b / (15 * I_b)$

$I_{c1} = \underline{\hspace{2cm}}$
 $I_{e1} = \underline{\hspace{2cm}}$

$I_{c2} = \underline{\hspace{2cm}}$
 $I_{e2} = \underline{\hspace{2cm}}$

$R_{sh} = \underline{\hspace{2cm}}$
 $h_{ie} = \underline{\hspace{2cm}}$
 (rbe)

$R_{sh} = \underline{\hspace{2cm}}$
 $h_{ie} = \underline{\hspace{2cm}}$
 (rbe)

$R1 = \underline{\hspace{2cm}}$
 $E_{R1} = \underline{\hspace{2cm}}$
 $I_{R1} = \underline{\hspace{2cm}}$

 $R2 = \underline{\hspace{2cm}}$
 $E_{R2} = \underline{\hspace{2cm}}$
 $I_{R2} = \underline{\hspace{2cm}}$

$R5 = \underline{\hspace{2cm}}$
 $E_{R5} = \underline{\hspace{2cm}}$
 $I_{R5} = \underline{\hspace{2cm}}$

 $R6 = \underline{\hspace{2cm}}$
 $E_{R6} = \underline{\hspace{2cm}}$
 $I_{R6} = \underline{\hspace{2cm}}$

Signal Limits = ____
 (SL1)
 $i_{o_pp} = \underline{\hspace{2cm}}$
 $e_{o_pp} = \underline{\hspace{2cm}}$
 $P(out) = \underline{\hspace{2cm}}$

 Actual SI = ____

Signal Limits = ____
 (SL2)
 $i_{o_pp} = \underline{\hspace{2cm}}$
 $e_{o_pp} = \underline{\hspace{2cm}}$
 $P(out) = \underline{\hspace{2cm}}$

 Actual SI = ____