

SAME LOGIC

<u>Positional Value:</u>	A	B	C	D	E	NAND GATE	OR GATE
	16	8	4	2	1		
0	0	0	0	0	0	???	1
1	0	0	0	0	1	???	1
2	0	0	0	1	0	???	1
3	0	0	0	1	1	???	1
4	0	0	1	0	0	???	1
5	0	0	1	0	1	???	1
6	0	0	1	1	0	0	
7	0	0	1	1	1	???	1
8	0	1	0	0	0	???	1
9	0	1	0	0	1	???	1
10	0	1	0	1	0	???	1
11	0	1	0	1	1	???	1
12	0	1	1	0	0	???	1
13	0	1	1	0	1	???	1
14	0	1	1	1	0	???	1
15	0	1	1	1	1	???	1
16	1	0	0	0	0	???	1
17	1	0	0	0	1	???	1
18	1	0	0	1	0	???	1
19	1	0	0	1	1	???	1
20	1	0	1	0	0	???	1
21	1	0	1	0	1	???	1
22	1	0	1	1	0	???	1
23	1	0	1	1	1	???	1
24	1	1	0	0	0	???	1
25	1	1	0	0	1	???	1
26	1	1	0	1	0	???	1
27	1	1	0	1	1	???	1
28	1	1	1	0	0	???	1
29	1	1	1	0	1	???	1
30	1	1	1	1	0	???	1
31	1	1	1	1	1	???	1