

Filter Considerations: (Outline:)

Special Note:

Since Filters involve Reactive Components, it would be well to discuss that aspect early.

Applications:

- Power Supplies
 - Removing the AC Component
 - Ripple Reduction
- Audio Circuits
 - Base Control
 - Treble Control
 - Hiss Reduction
 - Pass-Over-Unit" for Speakers
- Receivers (RF)
 - Tuning
 - IF Transformers"
- Transmitters
 - Carrier Generation
 - Sideband Control
- Oscillators
 - Audio (Tone)
 - VFO
 - BFO
 - MO
- Analysis
 - Spectral Analysis
 - Missile Telemetry
 - (Frequency and Energy Subjected to Missile Payloads)

General Types:

- Low-Pass
- High-Pass
- Bandpass
- Notch (Bandpass-Reject)

Configuration:

- L-Type
- T-Type
- Pi-Type
- Unbalanced
- Balanced

Uses:

- Signal Pass (Desired Signal)
- Signal Block (Undesired Signal)

Terminology:

Bandwidth
"Q"
Tuneable
Signal Loss
Quality Degredation
Resonant

Special Considerations:

Gamma-Match
Hairpin Tuning
Shorted Quarter-Wave Stub

Components:

Inductors
 Solid-Iron-Core
 Powdered Iron-Core
 Air-Core
 Transformer-Coupled
Capacitors (Elecrolytic and Non-Electrolytic)
Resistance

Special Types:

mDerived
Constant-K
Bessel
Butterworth
Tracking Filter