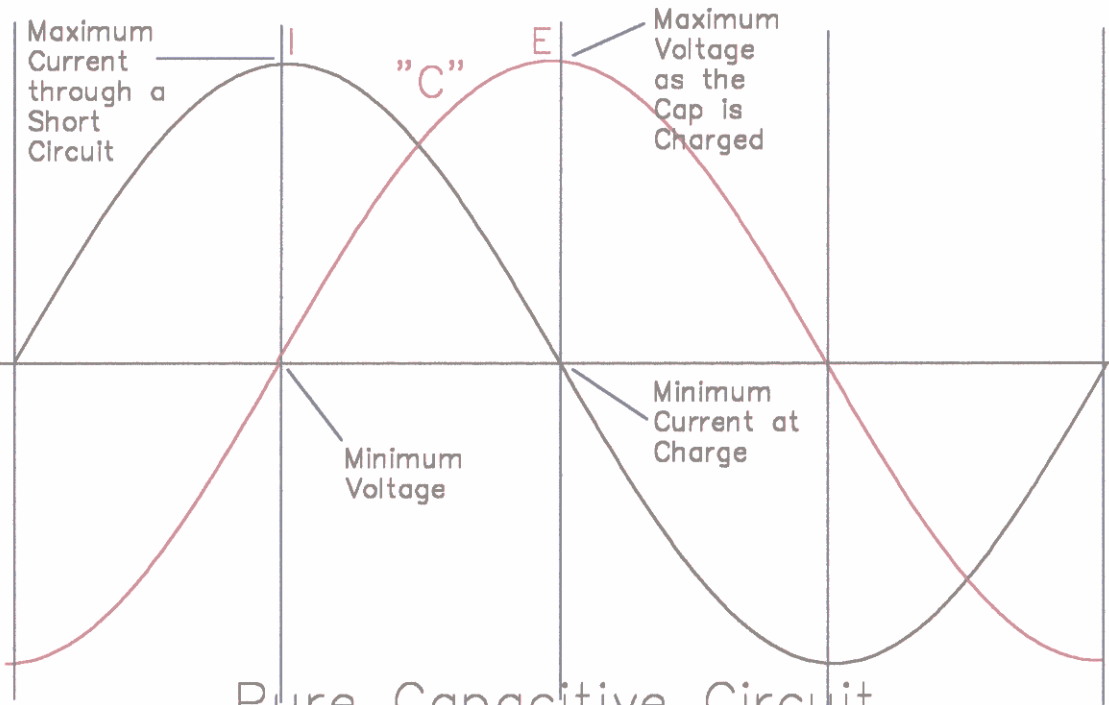


Maximum  
Current  
through a  
Short  
Circuit



"C"

E

Maximum  
Voltage  
as the  
Cap is  
Charged

Minimum  
Voltage

Minimum  
Current  
at  
Charge

Pure Capacitive Circuit